

2Ei5

Lab#4

Instructor: Dr. Haddara

Name: Yichen Lu

Student id: 400247938

Lab section: L01

Date: Feb. 20 th 2021


As a future member of the engineering profession, the student is responsible for performing the required work in an honest manner, without plagiarism and cheating. Submitting this work with my name and student number is a statement and understanding that this work is our own and adheres to the Academic Integrity Policy of McMaster University and the Code of Conduct of the Professional Engineers of Ontario. Submitted by Yichen Lu,luy191,400247938

Task1

Physical circuit




NPN output characteristic

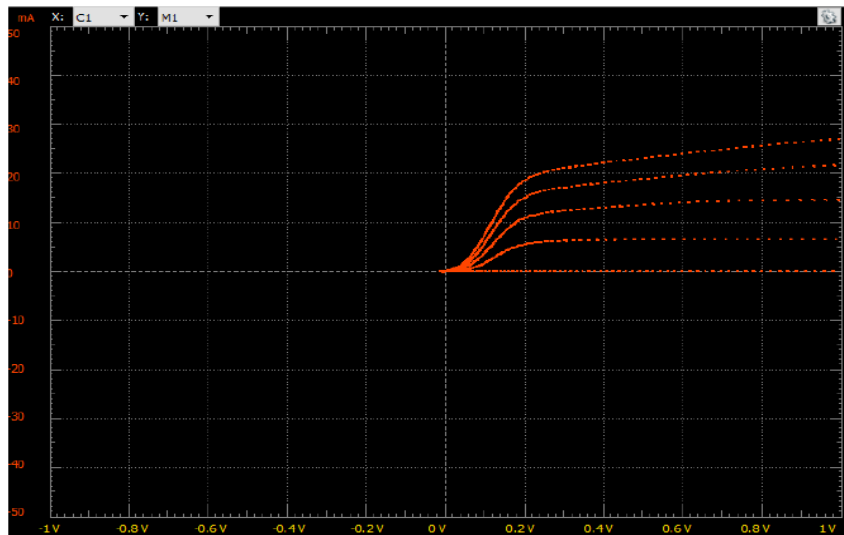


As we can see, VCE (sat) should be 0.2 V from this graph.

PNP output characteristic

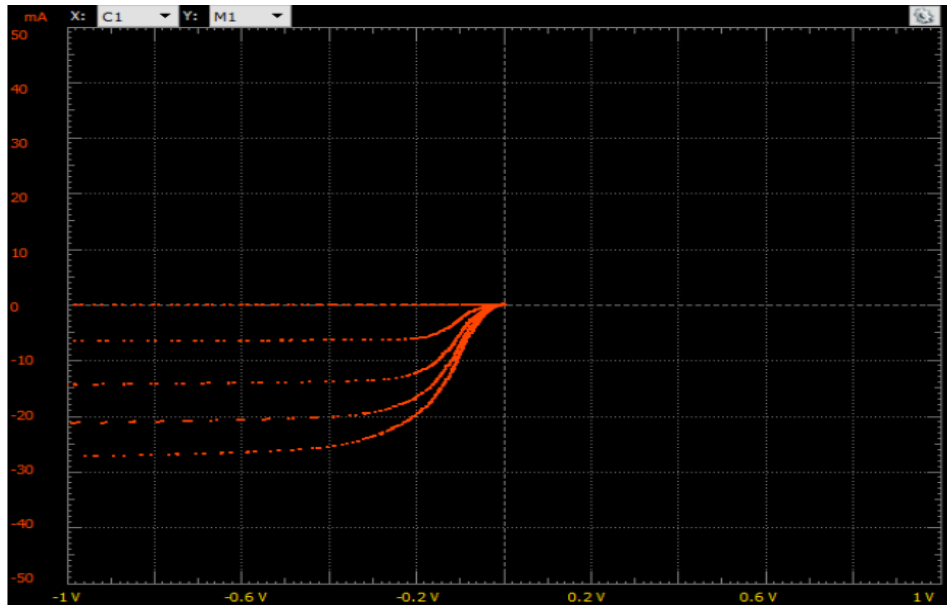


Task2

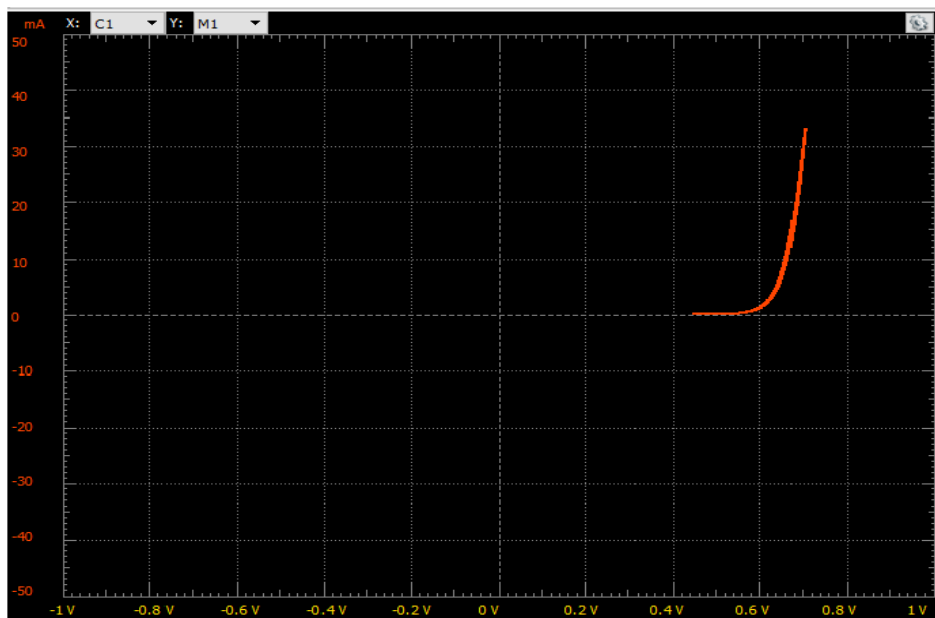

As we can see, VBE (on) should be 0.7v from the graph.
 β should be 100 by estimating.

Task3

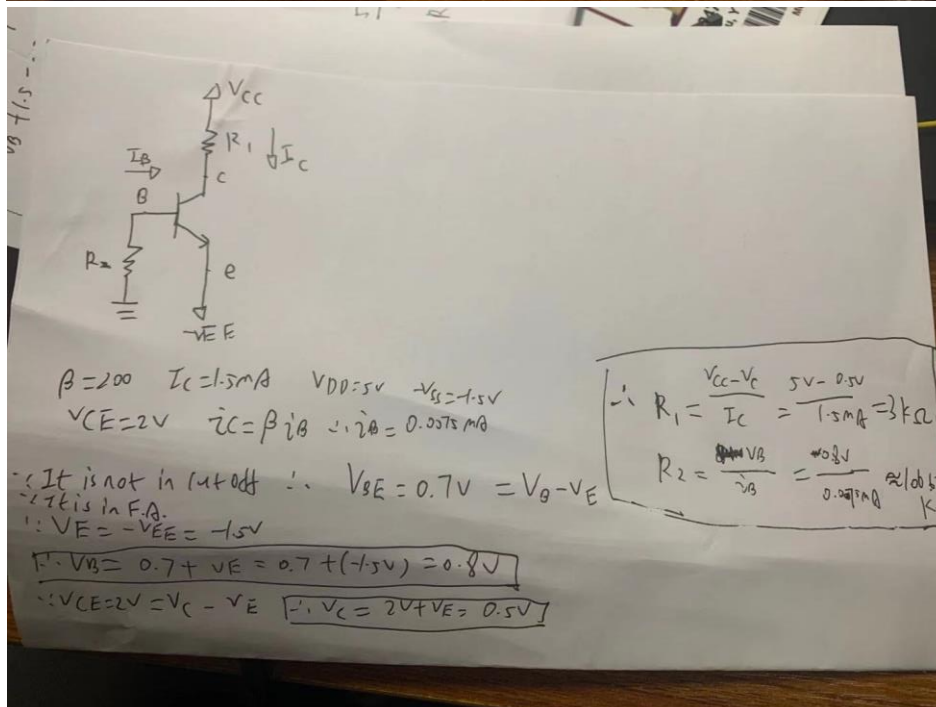

R1 is 3Kohm and R2 is 100Kohms.

2N3094

Channel 1	
DC	836 mV
True RMS	836 mV
AC RMS	0 V

Channel 2	
1.369 V	
1.369 \tilde{V}	
2 m \tilde{V}	

IC is around 2.1mA, and IB is around 8.3e-23A. β calculated is 254.


2N2222

Channel 1	
DC	-871 mV
True RMS	871 m \tilde{V}
AC RMS	1 m \tilde{V}

Channel 2	
-1.369 V	
1.369 \tilde{V}	
1 m \tilde{V}	

The result is similar with the above one. IC is about 2.1mA, and IB is about 8.71e-3mA. β calculated is 244.

Task4

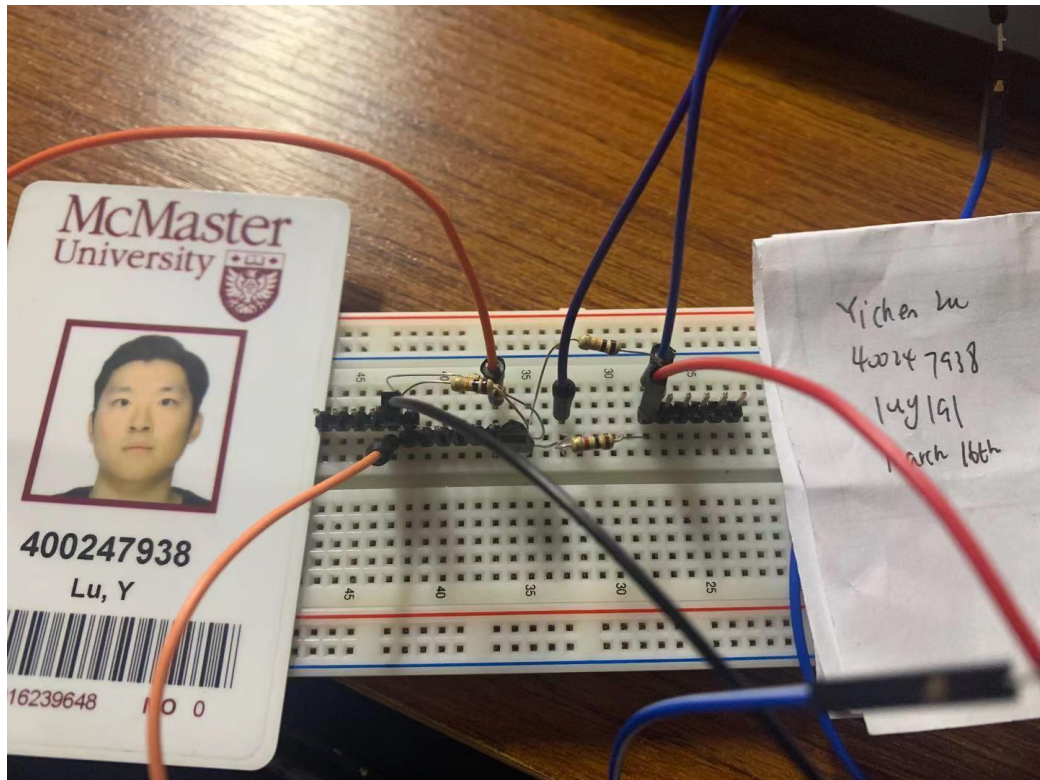

2N3094

Channel 1	
DC	-84 mV
True RMS	84 mV
AC RMS	2 mV

Channel 2	
754 mV	
754 mV	
1 mV	

IB is calculated 0.0167mA. IC is 4.28mA. β calculated is around 252.

2N2222

	Channel 1
DC	-85 mV
True RMS	85 mṼ
AC RMS	1 mṼ
	Channel 2
764 mV	
764 mṼ	
1 mṼ	

IB is calculated 0.0169mA. IC is 4.23mA. β calculated is around 249.